



Πανεπιστήμιο Δυτικής Αττικής

Σχολή Μηχανικών

Τμήμα Μηχανικών Πληροφορικής και Υπολογιστών

Σχεδίαση Ψηφιακών Συστημάτων

Θεωρία Τμήμα 2

Εξαμηνιαία Εργασία Μαθήματος - Υλοποίηση Επεξεργαστή MIPS

Αναστασία Αλμπάνη

Ice19390009

Εισαγωγή

Το κύκλωμα επεξεργαστή MIPS αποτελείται από τις μονάδες:


1. ALU
2. Register file
3. Μνήμη δεδομένων
4. Μνήμη εντολών
5. Μονάδα ελέγχου
6. Μονάδα ελέγχου ALU
7. PC
8. 5-πλό πολυπλέκτη 2-σε-1
9. Μονάδα επέκτασης προσήμου 16-σε-32

10, 11, 12. 32-πλό πολυπλέκτη 2-σε-1

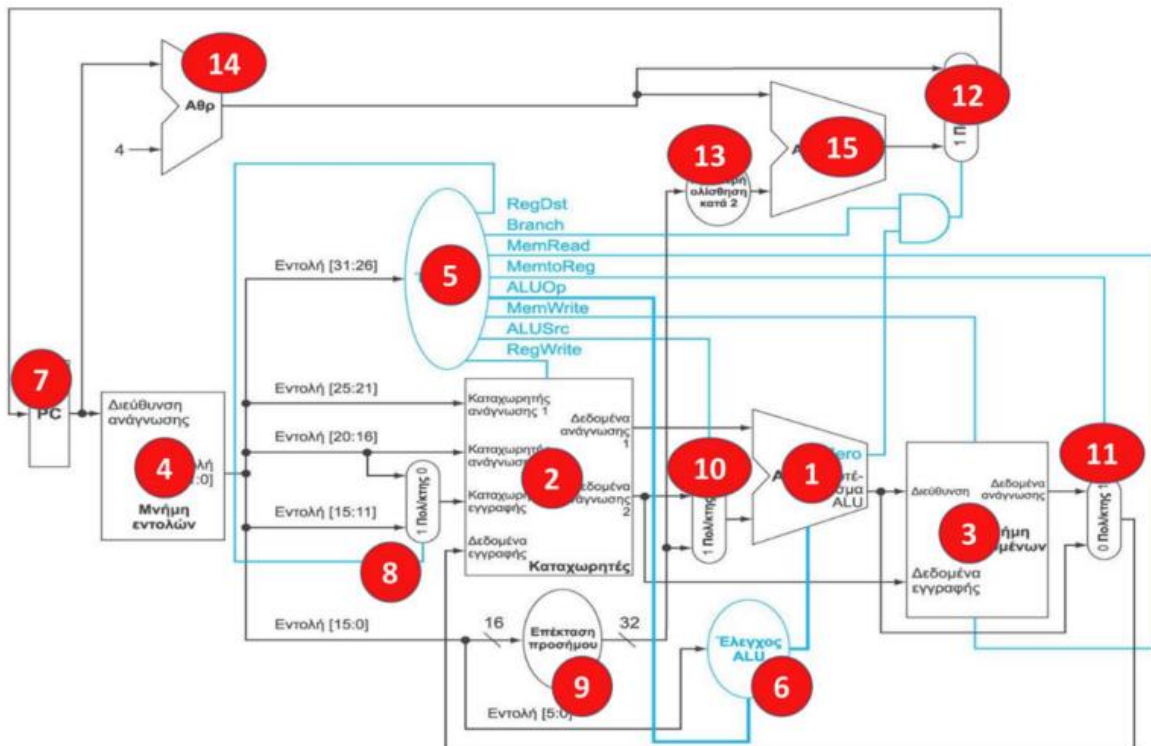13. Μονάδα ολίσθησης αριστερά κατά 2

14, 15. Αθροιστή 32 bits

Structural μονάδα MIPS η οποία συνδυάζει τις υπόλοιπες μονάδες



Οι εντολές οι οποίες υποστηρίζονται είναι: load word, store word, branch not equal, add, subtract, add immediate.

1. ALU

Το κύκλωμα ALU έχει δύο εισόδους δεδομένων και μία είσοδο operation η οποία ορίζει την πράξη των εισόδων. Η έξοδος alu_res είναι το αποτέλεσμα της πράξης και η έξοδος zero είναι ένα βοηθητικό σήμα που προσδιορίζει αν το αποτέλεσμα της εξόδου είναι μηδέν.

D1 (32 bit)	D2 (32 bit)	Operation	Alu resolution (32 bit)
X	X	0011 (addition)	D1 + D2
X	X	0110 (subtraction)	D1 - D2

Alu resolution (32 bit)	Zero
0	1
X	0

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;
USE IEEE.numeric_std.all;

entity ALU is port (
    -- ALU inputs
    D1 : in std_logic_vector(31 downto 0);
    D2 : in std_logic_vector(31 downto 0);
    operation : in std_logic_vector(3 downto 0);
    -- ALU outputs
    alu_res : out std_logic_vector(31 downto 0);
    zero : out std_logic
);
end ALU;

architecture behavioral of ALU is
```

```

        signal res : std_logic_vector(31 downto 0);

begin
    process(D1, D2, operation)
    begin
        case operation is
            -- addittion
            when "0011" =>
                res <= std_logic_vector(unsigned(D1) + unsigned(D2));
            -- subtract
            when "0110" =>
                res <= std_logic_vector(unsigned(D1) - unsigned(D2));
            when others => NULL;
        end case;
    end process;
    alu_res <= res;
    zero <= '1' when res = x"00000000" else
        '0';
end behavioral;

```

➤ Testbench

Το testbench ελέγχει πρώτα την πρόσθεση, μετά την αφαίρεση και τέλος την περίπτωση που το αποτέλεσμα της πράξης είναι 0.

- Κώδικας

```

library IEEE;
use IEEE.std_logic_1164.all;

```

```
entity ALU_tb is
end ALU_tb;
```

architecture test of ALU_tb is

```
    component ALU
```

```
    port (
```

```
        D1 : in std_logic_vector(31 downto 0);
```

```
        D2 : in std_logic_vector(31 downto 0);
```

```
        operation : in std_logic_vector(3 downto 0);
```

```
        alu_res : out std_logic_vector(31 downto 0);
```

```
        zero : out std_logic -- zero
```

```
    );
```

```
end component;
```

```
-- inputs
```

```
signal D1_tb : std_logic_vector(31 downto 0);
```

```
signal D2_tb : std_logic_vector(31 downto 0);
```

```
signal operation_tb : std_logic_vector(3 downto 0);
```

```
-- outputs
```

```
signal alu_res_tb : std_logic_vector(31 downto 0);
```

```
signal zero_tb : std_logic;
```

```
begin
```

```
    U1: ALU port map (
```

```
        D1 => D1_tb,
```

```
        D2 => D2_tb,
```

```

        operation => operation_tb,
        alu_res => alu_res_tb,
        zero => zero_tb);

-- stimulus process
process
begin

    -- addition
    D1_tb <= x"10101010";
    D2_tb <= x"01010101";
    operation_tb <= "0011";
    wait for 600 ns;


    -- subtract
    D1_tb <= x"55555555";
    D2_tb <= x"11111111";
    operation_tb <= "0110";
    wait for 600 ns;

    -- subtract equal
    D1_tb <= x"11111111";
    D2_tb <= x"11111111";
    operation_tb <= "0110";
    wait for 600 ns;

    -- runs for 1800 ns

end process;
end test;

```

 

2. Register file

Το κύκλωμα Register_file έχει δύο εισόδους καταχωρητών ανάγνωσης, μία είσοδο καταχωρητή εγγραφής η οποία έχει για τιμή την διεύθυνση στην οποία θα γίνει εγγραφή, μία είσοδο δεδομένων εγγραφής και εισόδους για ρολόι, reset και RegWrite. Το αρχείο καταχωρητών regfile έχει 16 θέσεις των 32 bit. Το reset είναι ασύγχρονο και όταν έχει τιμή '1' τότε μηδενίζονται τα δεδομένα των καταχωρητών. Όταν RegWrite = '1' τότε γίνεται η διαδικασία εγγραφής δεδομένων σε μία επιλεγμένη θέση καταχωρητή. Για εξόδους έχει τα δεδομένα των καταχωρητών των εισόδων ανάγνωσης.

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

entity register_file is port (
    -- number of address bits = 5
    rAddr1: in std_logic_vector(4 downto 0);
    rAddr2: in std_logic_vector(4 downto 0);
    wAddr : in std_logic_vector(4 downto 0);
    -- number of bits = 32
    wD : in std_logic_vector(31 downto 0);
    RegWrite : in std_logic;
    clk : in std_logic;
    reset : in std_logic;
    rD1 : out std_logic_vector(31 downto 0);
    rD2 : out std_logic_vector(31 downto 0));
end register_file;

architecture behavioral of register_file is
```



```

type regArray is array(0 to 15) of std_logic_vector(31 downto 0);

signal regfile : regArray;
begin
  process(clk, reset)
  begin
    -- reset
    if reset = '1' then
      regfile <= (others => (others => '0'));
    end if;
    if (clk'event and clk='1') then
      -- write to register
      if RegWrite='1' then
        regfile(to_integer(unsigned(wAddr))) <= wD;
      end if;
    end if;
  end process;
  -- read from register
  rD1 <= regfile(to_integer(unsigned(rAddr1)));
  rD2 <= regfile(to_integer(unsigned(rAddr2)));
end behavioral;

```

➤ Testbench

Στο testbench γίνεται reset και στη συνέχεια γράφονται δεδομένα σε όλες τις θέσεις των καταχωρητών. Τέλος διαβάζονται τα δεδομένα των καταχωρητών 2 και 3.

- Κώδικας

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY register_file_tb IS
END register_file_tb;

ARCHITECTURE test OF register_file_tb IS

    COMPONENT register_file PORT(
        rAddr1: in std_logic_vector(4 downto 0);
        rAddr2: in std_logic_vector(4 downto 0);
        wAddr : in std_logic_vector(4 downto 0);
        wD : in std_logic_vector(31 downto 0);
        RegWrite : in std_logic;
        clk : in std_logic;
        reset : in std_logic;
        rD1 : out std_logic_vector(31 downto 0);
        rD2 : out std_logic_vector(31 downto 0));
    END COMPONENT;

    -- inputs
    SIGNAL rAddr1_tb : std_logic_vector(4 downto 0);
    SIGNAL rAddr2_tb : std_logic_vector(4 downto 0);
    SIGNAL wAddr_tb : std_logic_vector(4 downto 0);
    SIGNAL wD_tb : std_logic_vector(31 downto 0);
    SIGNAL RegWrite_tb : std_logic;
```

```

    SIGNAL clk_tb : std_logic;
    SIGNAL reset_tb : std_logic;

    -- outputs
    SIGNAL rD1_tb : std_logic_vector(31 downto 0);
    SIGNAL rD2_tb : std_logic_vector(31 downto 0);

BEGIN

    U1: register_file PORT MAP (
        rAddr1 => rAddr1_tb,
        rAddr2 => rAddr2_tb,
        wAddr => wAddr_tb,
        wD => wD_tb,
        RegWrite => RegWrite_tb,
        clk => clk_tb,
        reset => reset_tb,
        rD1 => rD1_tb,
        rD2 => rD2_tb);

    -- clock process
    clk_p: PROCESS
    BEGIN
        clk_tb <= '1';
        WAIT FOR 300 ns;
        clk_tb <= '0';
        WAIT FOR 300 ns;
    END PROCESS clk_p;

    -- stimulus process

```

PROCESS

BEGIN

```
-- reset
reset_tb <= '1';
rAddr1_tb <= "00000";
rAddr2_tb <= "00000";
WAIT FOR 600 ns;

-- write to register
reset_tb <= '0';
RegWrite_tb <= '1';

wAddr_tb <= "00000";
wD_tb <= x"00000000";
WAIT FOR 600 ns;

wAddr_tb <= "00001";
wD_tb <= x"11111111";
WAIT FOR 600 ns;

wAddr_tb <= "00010";
wD_tb <= x"22222222";
WAIT FOR 600 ns;

wAddr_tb <= "00011";
wD_tb <= x"33333333";
WAIT FOR 600 ns;

wAddr_tb <= "00100";
wD_tb <= x"44444444";
```

```
WAIT FOR 600 ns;
```

```
wAddr_tb <= "00101";  
wD_tb <= x"55555555";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "00110";  
wD_tb <= x"66666666";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "00111";  
wD_tb <= x"77777777";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01000";  
wD_tb <= x"88888888";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01001";  
wD_tb <= x"99999999";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01010";  
wD_tb <= x"AAAAAAAA";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01011";  
wD_tb <= x"BBBBBBBB";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01100";  
wD_tb <= x"CCCCCCCC";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01101";  
wD_tb <= x"DDDDDDDD";  
WAIT FOR 600 ns;
```

```
wAddr_tb <= "01110";  
wD_tb <= x"EEEEEEEE";  
WAIT FOR 600 ns;
```


```
wAddr_tb <= "01111";  
wD_tb <= x"FFFFFFF";  
WAIT FOR 600 ns;
```

```
-- read from register  
RegWrite_tb <= '0';  
rAddr1_tb <= "00010";  
rAddr2_tb <= "00011";  
WAIT FOR 600 ns;
```

```
-- runs for 10800 ns
```

```
END PROCESS;
```

```
END test;
```

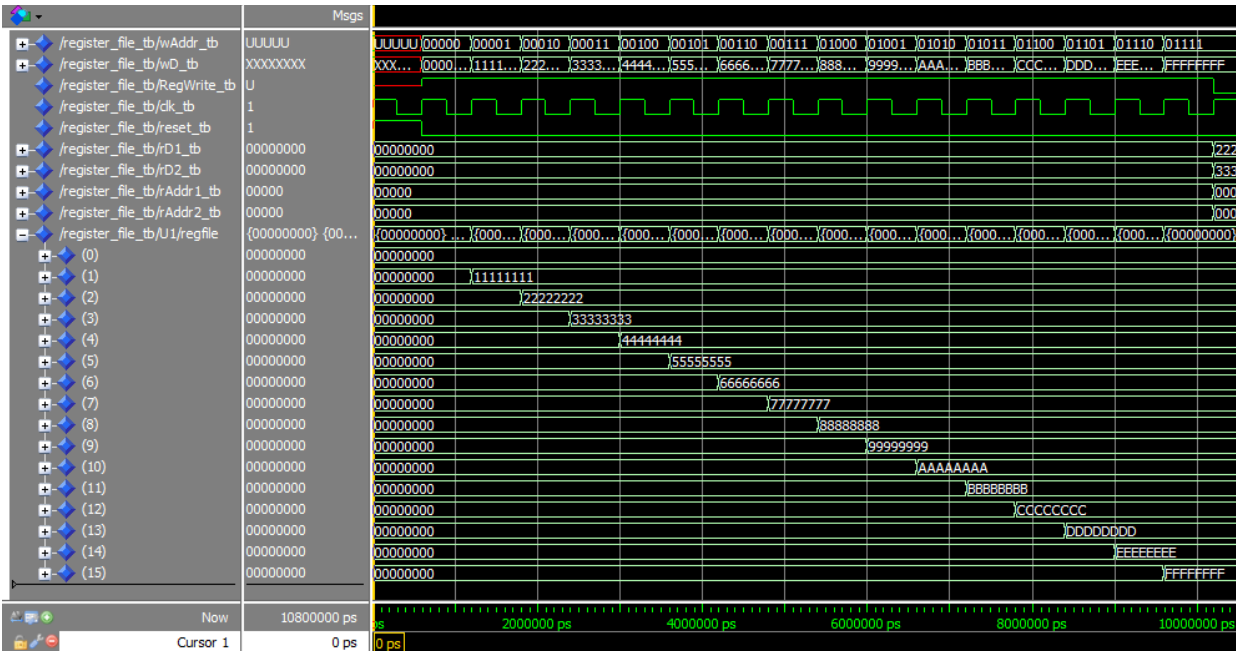

3. Μνήμη δεδομένων (Data memory)

Το κύκλωμα `data_memory` έχει για εισόδους μία διεύθυνση, τα δεδομένα εγγραφής και εισόδους για ρολόι, `reset`, `MemWrite` και `MemRead`. Για έξοδο έχει τα δεδομένα ανάγνωσης. Το αρχείο μνήμης δεδομένων `data_mem_file` έχει χωρητικότητα 16 θέσεων μνήμης των 32 bit. Το `reset` είναι ασύγχρονο και όταν έχει τιμή '1' τότε μηδενίζονται τα δεδομένα των καταχωρητών. Όταν `MemWrite = '1'` τότε γράφεται στην διεύθυνση τα δεδομένα εγγραφής και όταν `MemRead = '1'` τότε τα δεδομένα ανάγνωσης παίρνουν την τιμή των δεδομένων στην διεύθυνση.

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;
USE IEEE.numeric_std.all;

entity data_memory is port(
    -- data memory inputs
    address : in std_logic_vector(31 downto 0);
    write_data : in std_logic_vector(31 downto 0);
    clk : in std_logic;
    reset : in std_logic;
    MemWrite : in std_logic;
    MemRead : in std_logic;
    -- data memory output
    read_data : out std_logic_vector(31 downto 0)
);
end data_memory;

architecture behavioral of data_memory is

    type data_mem_array is array(0 to 15) of std_logic_vector(31 downto 0);
```



```

-- data memory file to zero
signal data_mem_file : data_mem_array := ((others => (others => '0')));
begin
  process(clk, reset)
  begin
    -- reset
    if reset = '1' then
      data_mem_file <= (others => (others => '0'));
    end if;

    -- clock
    if (clk'event and clk='1') then
      if (MemWrite = '1') then
        -- write data to address
        data_mem_file(to_integer(unsigned(address))) <=
          write_data;
      end if;

      if (MemRead = '1') then
        -- read data from address
        read_data <=
          data_mem_file(to_integer(unsigned(address)));
        else read_data <= x"00000000";
      end if;
    end if;
  end process;
end behavioral;

```

➤ Testbench

Στο testbench γίνεται reset και στη συνέχεια γράφονται δεδομένα σε όλους τους καταχωρητές. Τέλος διαβάζονται τα δεδομένα του καταχωρητή 10 και ξαναγίνεται reset.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity data_memory_tb is
end data_memory_tb;

architecture test of data_memory_tb is

    component data_memory
    port (
        address : in std_logic_vector(31 downto 0);
        write_data : in std_logic_vector(31 downto 0);
        clk : in std_logic;
        reset : in std_logic;
        MemWrite : in std_logic;
        MemRead : in std_logic;
        read_data : out std_logic_vector(31 downto 0)
    );
    end component;

    -- inputs
    signal address_tb : std_logic_vector(31 downto 0);
    signal write_data_tb : std_logic_vector(31 downto 0);
    signal MemWrite_tb : std_logic;
```

```

signal MemRead_tb : std_logic;
signal clk_tb : std_logic;
signal reset_tb : std_logic;

-- output
signal read_data_tb : std_logic_vector(31 downto 0);

begin
  U1: data_memory port map (
    address => address_tb,
    write_data => write_data_tb,
    clk => clk_tb,
    reset => reset_tb,
    MemWrite => MemWrite_tb,
    MemRead => MemRead_tb,
    read_data => read_data_tb);

  -- clock process
  clk_p: process
  begin
    clk_tb <= '1';
    wait for 300 ns;
    clk_tb <= '0';
    wait for 300 ns;
  end process clk_p;

  -- stimulus process
  process
  begin

```

```
-- reset
reset_tb <= '1';
wait for 600 ns;

-- write to data memory
reset_tb <= '0';
MemRead_tb <= '0';
MemWrite_tb <= '1';
address_tb <= x"00000000";
write_data_tb <= x"00000000";
wait for 600 ns;

address_tb <= x"00000001";
write_data_tb <= x"11111111";
wait for 600 ns;

address_tb <= x"00000002";
write_data_tb <= x"22222222";
wait for 600 ns;

address_tb <= x"00000003";
write_data_tb <= x"33333333";
wait for 600 ns;

address_tb <= x"00000004";
write_data_tb <= x"44444444";
wait for 600 ns;

address_tb <= x"00000005";
```

```
write_data_tb <= x"55555555";  
wait for 600 ns;
```

```
address_tb <= x"00000006";  
write_data_tb <= x"66666666";  
wait for 600 ns;
```

```
address_tb <= x"00000007";  
write_data_tb <= x"77777777";  
wait for 600 ns;
```

```
address_tb <= x"00000008";  
write_data_tb <= x"88888888";  
wait for 600 ns;
```

```
address_tb <= x"00000009";  
write_data_tb <= x"99999999";  
wait for 600 ns;
```

```
address_tb <= x"0000000A";  
write_data_tb <= x"AAAAAAAA";  
wait for 600 ns;
```

```
address_tb <= x"0000000B";  
write_data_tb <= x"BBBBBBBB";  
wait for 600 ns;
```

```
address_tb <= x"0000000C";  
write_data_tb <= x"CCCCCCCC";  
wait for 600 ns;
```

```

address_tb <= x"0000000D";
write_data_tb <= x"DDDDDDDD";
wait for 600 ns;

address_tb <= x"0000000E";
write_data_tb <= x"EEEEEEEE";
wait for 600 ns;


address_tb <= x"0000000F";
write_data_tb <= x"FFFFFFFF";
wait for 600 ns;

-- read from data memory
address_tb <= x"0000000A";
write_data_tb <= x"00000000";
MemRead_tb <= '1';
MemWrite_tb <= '0';
wait for 600 ns;

-- reset
reset_tb <= '1';
MemRead_tb <= '0';
MemWrite_tb <= '0';
wait for 600 ns;

-- runs for 11400 ns
end process;
end test;

```

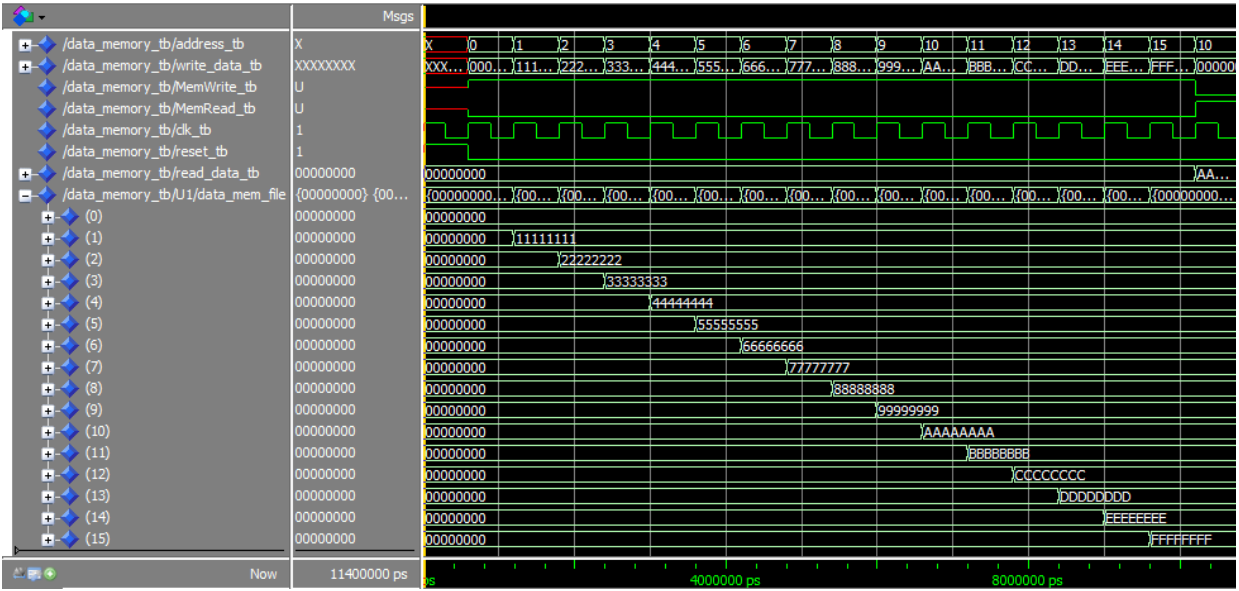

4. Μνήμη εντολών (Instruction memory)

Το κύκλωμα `instruction_memory` έχει για εισόδους την διεύθυνση ανάγνωσης, το ρολόι και το `reset`. Η έξοδος είναι η εντολή του επεξεργαστή η οποία διαβάζεται από τη διεύθυνση ανάγνωσης. Το αρχείο μνήμης εντολών `instr_mem_file` έχει χωρητικότητα 16 θέσεων μνήμης των 32 bit οι οποίες έχουν αποθηκευμένες της εντολές. Οι εντολές οι οποίες αποθηκεύονται είναι:

```
Addi $0, $0, 0
Addi $2, $2, 0
Addi $2, $4, 0
Addi $3, $0, 1
Addi $5, $0, 3
L1: add $6, $3, $0
    Sw $6, $3, $0
    Addi $3, $3, 1
    Addi $4, $4, 1
    Addi $5, $5, -1
Bne $5, $0, L1
```

Το `reset` είναι ασύγχρονο και όταν έχει τιμή '1' τότε μηδενίζεται η διεύθυνση ανάγνωσης για να αρχίσει το κύκλωμα να διαβάζει εντολές από την πρώτη θέση μνήμης.

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;
USE IEEE.numeric_std.all;

entity instruction_memory is port (
    -- MIPS inputs
```



```

    read_address : in std_logic_vector(31 downto 0);
    clk : in std_logic;
    reset: in std_logic;
    -- instruction memory output
    instruction : out std_logic_vector(31 downto 0)
);
end instruction_memory;

```

architecture behavioral of instruction_memory is

```

    type instr_mem_array is array(0 to 15) of std_logic_vector(31 downto
0);

    -- instruction memory initialization
    signal instr_mem_file : instr_mem_array := (
x"20000000", -- 0x0000 0000: addi $0, $0, 0
                (001000 00000 00000 00000 00000 000000)
x"20420000", -- 0x0000 0001: addi $2, $2, 0
                (001000 00010 00010 00000 00000 000000)
x"20820000", -- 0x0000 0002: addi $2, $4, 0
                (001000 00100 00010 00000 00000 000000)
x"20030001", -- 0x0000 0003: addi $3, $0, 1
                (001000 00000 00011 00000 00000 000001)
x"20050003", -- 0x0000 0004: addi $5, $0, 3
                (001000 00000 00101 00000 00000 000011)
x"00603020", -- 0x0000 0005: L1: add $6, $3, $0
                (000000 00011 00000 00110 00000 100000)
x"AC860000", -- 0x0000 0006: sw $6, 0($4)
                (101011 00100 00110 00000 00000 000000)
x"20630001", -- 0x0000 0007: addi $3, $3, 1

```

```

                                (001000 00011 00011 00000 00000 000001)
x"20840001", -- 0x0000 0008: addi $4, $4, 1
                                (001000 00100 00100 00000 00000 000001)
x"20A5FFFF", -- 0x0000 0009: addi $5, $5, -1
                                (001000 00101 00101 11111 11111 111111)
x"14A0FFF9", -- 0x0000 000A: bne $5, $0, L1
                                (000101 00101 00000 11111 11111 111001)

x"00000000",
x"00000000",
x"00000000",
x"00000000",
x"00000000");

```

```

begin
    process(clk, reset)
    begin
        if (reset = '1') then
            instruction <= x"00000000";
        end if;
        if (clk'event and clk='1') then
            instruction <=
            instr_mem_file(to_integer(unsigned(read_address)));
        end if;
    end process;
end behavioral;

```

➤ Testbench

Στο testbench γίνεται reset και στη συνέχεια διαβάζονται όλοι οι καταχωρητές της μνήμης εντολών.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity instruction_memory_tb is
end instruction_memory_tb;

architecture test of instruction_memory_tb is

    component instruction_memory
    port (
        read_address : in std_logic_vector(31 downto 0);
        clk : in std_logic;
        reset: in std_logic;
        instruction : out std_logic_vector(31 downto 0)
    );
    end component;

    -- inputs
    signal read_address_tb : std_logic_vector(31 downto 0);
    signal clk_tb : std_logic;
    signal reset_tb : std_logic;

    -- output
    signal instruction_tb : std_logic_vector(31 downto 0);

begin
```

```

U1: instruction_memory port map (
    read_address => read_address_tb,
    clk => clk_tb,
    reset => reset_tb,
    instruction => instruction_tb);

-- clock process
clk_p: process
begin
    clk_tb <= '1';
    wait for 300 ns;
    clk_tb <= '0';
    wait for 300 ns;
end process clk_p;

-- stimulus process
process
begin
    -- reset
    reset_tb <= '1';
    wait for 600 ns;

    -- read instruction
    reset_tb <= '0';
    read_address_tb <= x"00000000";
    wait for 600 ns;

    read_address_tb <= x"00000001";
    wait for 600 ns;

```

```
read_address_tb <= x"00000002";  
wait for 600 ns;
```

```
read_address_tb <= x"00000003";  
wait for 600 ns;
```

```
read_address_tb <= x"00000004";  
wait for 600 ns;
```

```
read_address_tb <= x"00000005";  
wait for 600 ns;
```

```
read_address_tb <= x"00000006";  
wait for 600 ns;
```


```
read_address_tb <= x"00000007";  
wait for 600 ns;
```


```
read_address_tb <= x"00000008";  
wait for 600 ns;
```

```
read_address_tb <= x"00000009";  
wait for 600 ns;
```

```
read_address_tb <= x"0000000A";  
wait for 600 ns;
```
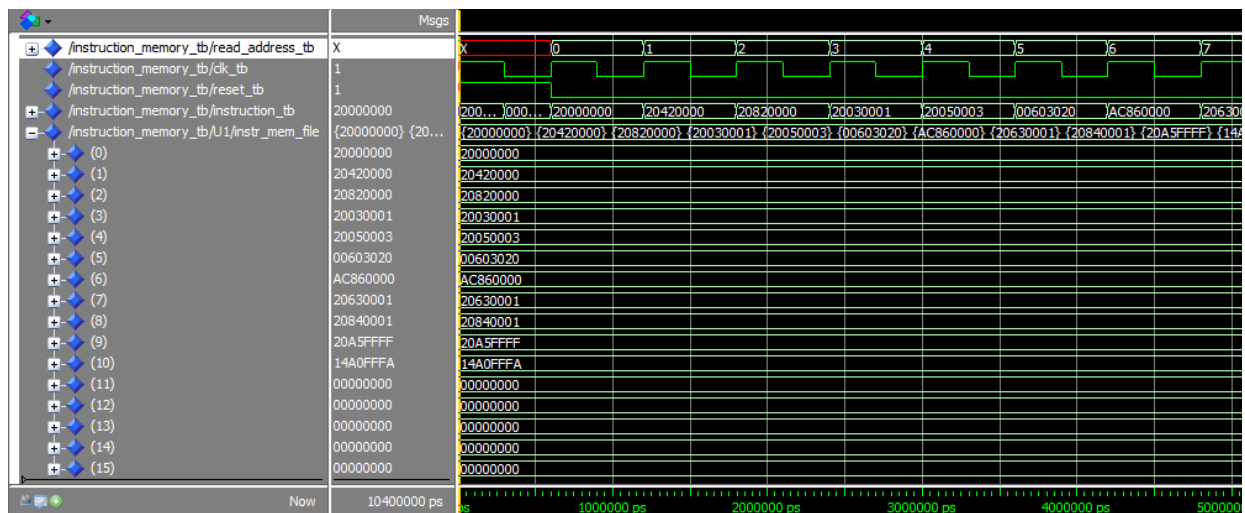
```
read_address_tb <= x"0000000B";  
wait for 600 ns;
```



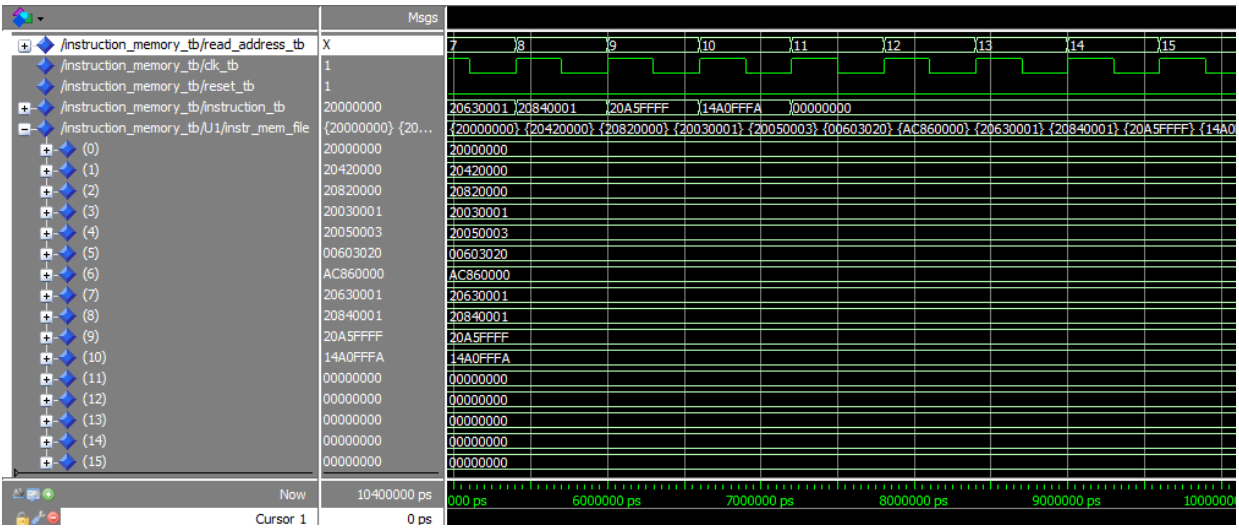

5. Μονάδα ελέγχου (Control unit)

Το κύκλωμα `control_unit` έχει για είσοδο τον κώδικα διαδικασίας και για εξόδους τα σήματα `RegDst`, `Branch`, `MemRead`, `MemtoReg`, `ALUOp`, `MemWrite`, `ALUSrc` και `RegWrite`.

Εντολή	opcode	Reg Dst	Branch	Mem Read	Memto Reg	ALUOp	Mem Write	ALUSrc	RegWrite
load word	100011	0	0	1	1	00	0	1	1
store word	101011	X	0	0	X	00	1	1	0
branch not equal	000101	X	1	0	X	01	0	0	0
add	000000	1	0	0	0	10	0	0	1
subtract	000000	1	0	0	0	10	0	0	1
add immediate	001000	0	0	0	0	11	0	1	1

- Κώδικας

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity control_unit is port (
```

```
-- operation code for 31-26 of instruction memory
```

```
opcode : in std_logic_vector(5 downto 0);
```

```
-- control signals of operation
```

```
RegDst : out std_logic;
```

```
Branch : out std_logic;
```

```
MemRead : out std_logic;
```

```
MemtoReg : out std_logic;
```

```
ALUOp : out std_logic_vector(1 downto 0);
```

```
MemWrite : out std_logic;
```

```
ALUSrc : out std_logic;
```

```
RegWrite : out std_logic
```



```
);  
end control_unit;
```

architecture behavioral of control_unit is

```
begin  
  process(opcode)  
  Begin  
    case opcode is  
      -- Register type instructions : and, sub  
      when "000000" =>  
        RegDst <= '1'; -- register address 15-11 to write  
        Branch <= '0';  
        MemRead <= '0';  
        MemtoReg <= '0';  
        ALUOp <= "10";  
        MemWrite <= '0';  
        ALUSrc <= '0';  
        RegWrite <= '1'; -- write data to register address  
      -- Immediate type instructions  
      when "001000" => -- addi (add immediate word)  
        RegDst <= '0'; -- register address 20-16 to write  
        Branch <= '0';  
        MemRead <= '0';  
        MemtoReg <= '0';  
        ALUOp <= "11";  
        MemWrite <= '0';  
        ALUSrc <= '1'; -- alu uses integer value 15-0  
        RegWrite <= '1'; -- write data to register address  
      when "100011" => -- lw (load word)  
        RegDst <= '0';
```

```

        Branch <= '0';
        MemRead <= '1'; -- read from data memory
        MemtoReg <= '1';
        ALUOp <= "00";
        MemWrite <= '0';
        ALUSrc <= '1'; -- alu uses offset value 15-0
        RegWrite <= '1'; -- write data to register address
    when "101011" => -- sw (store word)
        RegDst <= 'X';
        Branch <= '0';
        MemRead <= '0';
        MemtoReg <= 'X';
        ALUOp <= "00";
        MemWrite <= '1'; -- write to data memory
        ALUSrc <= '1'; -- alu uses offset value 15-0
        RegWrite <= '0';
    when "000101" => -- bne (branch not equal)
        RegDst <= 'X';
        Branch <= '1'; -- add value to program counter
        MemRead <= '0';
        MemtoReg <= 'X';
        ALUOp <= "01";
        MemWrite <= '0';
        ALUSrc <= '0';
        RegWrite <= '0';
    when others => NULL;
end case;
end process;
end behavioral;

```

➤ Testbench

Στο testbench ελέγχονται τα σήματα του control unit για τις εντολές add και sub, addi, lw, sw και bne.

- Κώδικας

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY control_unit_tb IS
END control_unit_tb;

ARCHITECTURE test OF control_unit_tb IS

COMPONENT control_unit PORT(
    opcode : in std_logic_vector(5 downto 0);
    RegDst : out std_logic;
    Branch : out std_logic;
    MemRead : out std_logic;
    MemtoReg : out std_logic;
    ALUOp : out std_logic_vector(1 downto 0);
    MemWrite : out std_logic;
    ALUSrc : out std_logic;
    RegWrite : out std_logic);
END COMPONENT;

-- input
SIGNAL opcode_tb : std_logic_vector(5 downto 0);
```

```
-- outputs
SIGNAL RegDst_tb : std_logic;
SIGNAL Branch_tb : std_logic;
SIGNAL MemRead_tb : std_logic;
SIGNAL MemtoReg_tb : std_logic;
SIGNAL ALUOp_tb : std_logic_vector(1 downto 0);
SIGNAL MemWrite_tb : std_logic;
SIGNAL ALUSrc_tb : std_logic;
SIGNAL RegWrite_tb : std_logic;
```

```
BEGIN
```

```
U1: control_unit PORT MAP (
opcode => opcode_tb,
RegDst => RegDst_tb,
Branch => Branch_tb,
MemRead => MemRead_tb,
MemtoReg => MemtoReg_tb,
ALUOp => ALUOp_tb,
MemWrite => MemWrite_tb,
ALUSrc => ALUSrc_tb,
RegWrite => RegWrite_tb);
```

```
-- stimulus process
```

```
PROCESS
```

```
BEGIN
```

```
-- add, sub
```

```
opcode_tb <= "000000";
```

```
WAIT FOR 600 ns;
```

```

-- addi
opcode_tb <= "001000";
WAIT FOR 600 ns;

-- lw (load word)
opcode_tb <= "100011";
WAIT FOR 600 ns;

-- sw (store word)
opcode_tb <= "101011";
WAIT FOR 600 ns;


-- bne (branch not equal)
opcode_tb <= "000101";
WAIT FOR 600 ns;

-- runs for 3000 ns

END PROCESS;

END test;

```

 

6. Μονάδα ελέγχου ALU

Το κύκλωμα `ALU_control` έχει για είσοδο το σήμα `ALUop` και το τμήμα `funct` της εντολής του επεξεργαστή και επιστρέφει στην ALU το operation το οποίο καθορίζει αν θα γίνει πρόσθεση ή αφαίρεση. Για πρόσθεση το operation είναι 0011 και για αφαίρεση είναι 0110.

Εντολή	Τύπος εντολής	funct	Aluop	Operation
load word	I	xxxxxx	00	0011
store word	I	xxxxxx	00	0011
branch not equal	I	xxxxxx	01	0110
add	R	100000	10	0011
subtract	R	100010	10	0110
add immediate	I	xxxxxx	11	0011

- Κώδικας

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity ALU_control is port (
```

```
-- operation and function for ALU
```

```
ALUop : in std_logic_vector(1 downto 0);
```

```
funct : in std_logic_vector(5 downto 0);
```

```
-- ALU operation
```

```
operation : out std_logic_vector(3 downto 0)
```

```
);
```

```
end ALU_control;
```

```
architecture behavioral of ALU_control is
```

```

begin
  process(ALUop, funct)
  Begin
    if ALUop = "01" then          -- branch not equal
      operation <= "0110";
    elsif ALUop = "10" then
      if funct = "100000" then    -- add
        operation <= "0011";
      elsif funct = "100010" then -- subtract
        operation <= "0110";
      end if;
    elsif ALUop = "11" then      -- add immediate
      operation <= "0011";
    else -- ALUop = "00"
      operation <= "0011";      -- load word and store word
    end if;
  end process;
end behavioral;

```

➤ Testbench

Στο testbench ελέγχεται το operation για τα ALUop, funct των εντολών lw, sw, bne, add, sub και addi.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ALU_control_tb is
end ALU_control_tb;

architecture test of ALU_control_tb is

    component ALU_control
    port (
        ALUop : in std_logic_vector(1 downto 0);
        funct : in std_logic_vector(5 downto 0);
        operation : out std_logic_vector(3 downto 0)
    );
    end component;

    -- inputs
    signal ALUop_tb : std_logic_vector(1 downto 0);
    signal funct_tb : std_logic_vector(5 downto 0);

    -- output
    signal operation_tb : std_logic_vector(3 downto 0);

begin

    U1: ALU_control port map (
        ALUop => ALUop_tb,
```



```

    funct => funct_tb,
    operation => operation_tb);

-- stimulus process
process
begin

    -- load word and store word
    ALUop_tb <= "00";
    funct_tb <= "000000";
    wait for 600 ns;

    -- branch not equal
    ALUop_tb <= "01";
    funct_tb <= "100000";
    wait for 600 ns;

    -- add
    ALUop_tb <= "10";
    funct_tb <= "100010";
    wait for 600 ns;

    -- subtract
    ALUop_tb <= "10";
    funct_tb <= "100100";
    wait for 600 ns;

    -- addi
    ALUop_tb <= "11";
    funct_tb <= "000000";


```

```
wait for 600 ns;
```

```
-- runs for 3000 ns
```

```
end process;
```

```
end test;
```

 

7. PC

Το κύκλωμα PC έχει για είσοδο την διεύθυνση ανάγνωσης, το ρολόι και το reset και για έξοδο την διεύθυνση ανάγνωσης της εισόδου. Συγχρονίζει με βάση το ρολόι το διάβασμα της διεύθυνσης στη μνήμη εντολών. Το reset είναι ασύγχρονο και όταν έχει τιμή '1' τότε θέτει τη διεύθυνση σε x00000000.

PCin (32 bit)	reset	PCout (32 bit)
XXXXXXXX	0	PCin
XXXXXXXX	1	x00000000

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;

entity PC is port (
    -- PC inputs
    PCin : in std_logic_vector(31 downto 0);
    reset : in std_logic;
    clk : in std_logic;
    -- PC output
    PCout : out std_logic_vector(31 downto 0)
);
end PC;

architecture behavioral of PC is
    signal pout: std_logic_vector(31 downto 0);

begin
    process(clk, reset)
    begin
```

```

        if reset = '1' then
            pout <= x"00000000";
        end if;
        if (clk'event and clk='1') then
            pout <= PCin;
        end if;
    end process;
    PCout <= pout;
end behavioral;

```

➤ Testbench

Στο testbench ελέγχεται το reset και το PCout για PCin ίσο με x00000001 και x00000002.

- Κώδικας

```

library IEEE;
use IEEE.std_logic_1164.all;

entity PC_tb is
end PC_tb;

architecture test of PC_tb is

    component PC
    port (
        PCin : in std_logic_vector(31 downto 0);
        reset : in std_logic;

```

```

    clk : in std_logic;
    PCout : out std_logic_vector(31 downto 0)
);
end component;

-- inputs
signal PCin_tb : std_logic_vector(31 downto 0);
signal reset_tb : std_logic;
signal clk_tb : std_logic;

-- output
signal PCout_tb : std_logic_vector(31 downto 0);

begin
    U1: PC port map (
        PCin => PCin_tb,
        reset => reset_tb,
        clk => clk_tb,
        PCout => PCout_tb);

    -- clock process
clk_p: process
begin
    clk_tb <= '1';
    wait for 300 ns;
    clk_tb <= '0';
    wait for 300 ns;
end process clk_p;

```

```

-- stimulus process
process
begin

    reset_tb <= '1';
    wait for 600 ns;


    reset_tb <= '0';
    PCin_tb <= x"00000001";
    wait for 600 ns;

    PCin_tb <= x"00000002";
    wait for 600 ns;

    -- runs for 1800 ns

end process;
end test;

```

 

8. 5-πλός Πολυπλέκτης 2-σε-1

Το κύκλωμα `mux2to1_5bit` έχει δύο εισόδους 5 bit, μία είσοδο `select` και μία έξοδο 5 bit η οποία ανάλογα με την τιμή της `select` παίρνει την τιμή μίας εισόδου.

A1 (5 bit)	A2 (5 bit)	s	D (5 bit)
XXXXX	XXXXX	1	A1
XXXXX	XXXXX	0	A2

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux2to1_5bit is port (
    a1: in std_logic_vector(4 downto 0);
    a2: in std_logic_vector(4 downto 0);
    s : in std_logic;
    d: out std_logic_vector(4 downto 0)
);
end mux2to1_5bit;

architecture dataflow of mux2to1_5bit is
begin
    d <= a1 when s = '1' else
        a2;
end dataflow;
```

➤ Testbench

Στο testbench ελέγχεται η έξοδος για τις εισόδους 00000 και 11111 με select ίσο με 0 και 1.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux2to1_5bit_tb is
end mux2to1_5bit_tb;

architecture test of mux2to1_5bit_tb is

    -- mux2to1 5 bit
    component mux2to1_5bit
    port (
        a1: in std_logic_vector(4 downto 0);
        a2: in std_logic_vector(4 downto 0);
        s : in std_logic;
        d: out std_logic_vector(4 downto 0)
    );
    end component;

    -- inputs
    signal a1_tb, a2_tb: std_logic_vector(4 downto 0) := (others => '0');
    signal s_tb : std_logic := '0';

    -- outputs
```



```

    signal d_tb: std_logic_vector(4 downto 0);

begin

    U1: mux2to1_5bit port map (
        a1 => a1_tb,
        a2 => a2_tb,
        s  => s_tb,
        d  => d_tb);


    -- stimulus process
    process
    begin

        a1_tb <= "00000";
        a2_tb <= "11111";
        s_tb  <= '0';
        wait for 300 ns;

        s_tb <= '1';
        wait for 300 ns;

    end process;
end test;

```

 

9. Μονάδα επέκτασης προσήμου 16-σε-32 (Sign Extender)

Το κύκλωμα `sign_extender` έχει μία είσοδο 16 bit και την μετατρέπει σε 32 bit ανάλογα με το πρόσημο της.

Sin (16 bit)	Sout (32 bit)
<code>sin(15) = '0'</code>	<code>x"0000" & Sin</code>
<code>sin(15) = '1'</code>	<code>X"FFFF" & Sin</code>

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_signed.all;

entity sign_extender is port (
    sin : in std_logic_vector(15 downto 0);
    sout: out std_logic_vector(31 downto 0));
end sign_extender;

architecture dataflow of sign_extender is
begin
    sout(31 downto 0) <= x"0000" & sin(15 downto 0) when sin(15) = '0' else
        x"ffff" & sin(15 downto 0);
end dataflow;
```

➤ Testbench

Στο testbench ελέγχεται η έξοδος για είσοδο με πρόσημοα '1' και '0'.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity sign_extender_tb is
end sign_extender_tb;

architecture test of sign_extender_tb is

    -- sign extender 32 bit
    component sign_extender
    port (
        sin : in std_logic_vector(15 downto 0);
        sout: out std_logic_vector(31 downto 0)
    );
    end component;

    -- input
    signal sin_tb: std_logic_vector(15 downto 0) := (others => '0');

    -- output
    signal sout_tb: std_logic_vector(31 downto 0);

begin

    U1: sign_extender port map (
```

```

sin => sin_tb,
sout => sout_tb);


-- stimulus process
process
begin

    sin_tb <= x"FFFF";
    wait for 300 ns;

    sin_tb <= x"0000";
    wait for 300 ns;

end process;
end test;

```

 

10. 32-πλός Πολυπλέκτης 2-σε-1

Το κύκλωμα `mux2to1_32bit` έχει δύο εισόδους 32 bit, μία είσοδο `select` και μία έξοδο 32 bit η οποία ανάλογα με την τιμή της `select` παίρνει την τιμή μίας εισόδου.

A1 (32 bit)	A2 (32 bit)	s	D (32 bit)
X"XXXXXXXX"	X"XXXXXXXX"	1	A1
X"XXXXXXXX"	X"XXXXXXXX"	0	A2

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux2to1_32bit is port (
    a1: in std_logic_vector(31 downto 0);
    a2: in std_logic_vector(31 downto 0);
    s : in std_logic;
    d: out std_logic_vector(31 downto 0)
);
end mux2to1_32bit;

architecture dataflow of mux2to1_32bit is
begin
    d <= a1 when s = '1' else
        a2;
end dataflow;
```

➤ Testbench

Στο testbench ελέγχεται η έξοδος για τις εισόδους x00001111 και x11110000 με select ίσο με 0 και 1.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux2to1_32bit_tb is
end mux2to1_32bit_tb;

architecture test of mux2to1_32bit_tb is

    -- mux2to1 32 bit
    component mux2to1_32bit
    port (
        a1: in std_logic_vector(31 downto 0);
        a2: in std_logic_vector(31 downto 0);
        s : in std_logic;
        d: out std_logic_vector(31 downto 0)
    );
    end component;

    -- inputs
    signal a1_tb, a2_tb: std_logic_vector(31 downto 0) := (others => '0');
    signal s_tb : std_logic := '0';
```

```

-- outputs
signal d_tb: std_logic_vector(31 downto 0);

begin
  U1: mux2to1_32bit port map (
    a1 => a1_tb,
    a2 => a2_tb,
    s  => s_tb,
    d  => d_tb);


-- stimulus process
process
  begin

    a1_tb <= x"00001111";
    a2_tb <= x"11110000";
    s_tb  <= '0';
    wait for 300 ns;

    s_tb <= '1';
    wait for 300 ns;

  end process;
end test;

```

 

11. Μονάδα ολίσθησης αριστερά κατά 2 (32 bit) (Shift left)

Το κύκλωμα `shift_left2_32bit` έχει μία είσοδο 32 bit και ολισθαίνει την τιμή της αριστερά κατά 2 μηδενικά bit.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_signed.all;

entity shift_left2_32bit is port (
    sin : in std_logic_vector(31 downto 0);
    sout: out std_logic_vector(31 downto 0));
end shift_left2_32bit;

architecture dataflow of shift_left2_32bit is
begin
    sout(31 downto 0) <= sin(29 downto 0) & "00";
end dataflow;
```

➤ Testbench

Στο testbench ελέγχεται η έξοδος για είσοδο `x11111111` και `xFFFFFFFF`.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity shift_left2_32bit_tb is
end shift_left2_32bit_tb;

architecture test of shift_left2_32bit_tb is

    -- shift left by 2 32 bit
    component shift_left2_32bit
    port (
        sin : in std_logic_vector(31 downto 0);
        sout: out std_logic_vector(31 downto 0)
    );
    end component;

    -- input
    signal sin_tb: std_logic_vector(31 downto 0);

    -- output
    signal sout_tb: std_logic_vector(31 downto 0);

begin

    U1: shift_left2_32bit port map (
        sin => sin_tb,
        sout => sout_tb);
```

```
end test;
```



12. Αθροιστής 32 bit (Adder)

Το κύκλωμα `adder_32bit` έχει δύο εισόδους 32 bit και μία έξοδο η οποία είναι το άθροισμα τους.

A (32 bit)	B (32 bit)	Cout (32 bit)
x"XXXXXXXX"	x"XXXXXXXX"	A + B

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_signed.all;

entity adder_32bit is port (
    a, b : in std_logic_vector(31 downto 0);
    cout: out std_logic_vector(31 downto 0));
end adder_32bit;

architecture dataflow of adder_32bit is
begin
    cout(31 downto 0) <= a(31 downto 0) + b(31 downto 0);
end dataflow;
```

➤ Testbench

Στο testbench ελέγχεται η έξοδος για εισόδους με αριθμούς x22222222,x11111111 και x22222222, x33333333.

- Κώδικας

```
library IEEE;
use IEEE.std_logic_1164.all;

entity adder_32bit_tb is
end adder_32bit_tb;

architecture test of adder_32bit_tb is

    -- adder 32 bit
    component adder_32bit
    port (
        a, b : in std_logic_vector(31 downto 0);
        cout: out std_logic_vector(31 downto 0)
    );
    end component;

    -- inputs
    signal a_tb, b_tb: std_logic_vector(31 downto 0) := (others => '0');

    -- outputs
    signal cout_tb: std_logic_vector(31 downto 0);

begin

    U1: adder_32bit port map (
        a => a_tb,
```

```

        b => b_tb,
        cout => cout_tb);


-- stimulus process
process
begin

    a_tb <= x"22222222";
    b_tb <= x"11111111";
    wait for 600 ns;

    a_tb <= x"33333333";
    b_tb <= x"22222222";
    wait for 600 ns;

end process;
end test;

```

 

13.MIPS

Το κύκλωμα MIPS χρησιμοποιεί ως component όλα τα προηγούμενα κυκλώματα εκτός από τη μονάδα ολίσθησης αριστερά διότι το PC αυξάνεται κατά 1 και δεν χρειάζεται να γίνει πολλαπλασιασμός του offset. Τα κυκλώματα συνδυάζονται σύμφωνα με την πρώτη εικόνα.

Για την εντολή bne χρησιμοποιείται μια πύλη and με εισόδους το σήμα Branch και την άρνηση του zero.

- Κώδικας

```
library ieee;
use ieee.std_logic_1164.all;

entity MIPS is port (
-- MIPS inputs
reset : in std_logic;
clk : in std_logic
);
end MIPS;

architecture structural of MIPS is

    signal MIPS_clk : std_logic;
    signal MIPS_reset : std_logic;

-- 1. ALU component
    component ALU
    port (
        D1 : in std_logic_vector(31 downto 0);
        D2 : in std_logic_vector(31 downto 0);
```

```

    operation : in std_logic_vector(3 downto 0);
    alu_res : out std_logic_vector(31 downto 0);
    zero : out std_logic); -- zero
end component;

-- ALU inputs and outputs
signal ALU_D1 : std_logic_vector(31 downto 0);
signal ALU_D2 : std_logic_vector(31 downto 0);
signal ALU_alu_res : std_logic_vector(31 downto 0);
signal ALU_zero : std_logic;

-- 2. Register file component
component register_file
port (
    rAddr1: in std_logic_vector(4 downto 0);
    rAddr2: in std_logic_vector(4 downto 0);
    wAddr : in std_logic_vector(4 downto 0);
    wD : in std_logic_vector(31 downto 0);
    RegWrite : in std_logic;
    clk : in std_logic;
    reset : in std_logic;
    rD1 : out std_logic_vector(31 downto 0);
    rD2 : out std_logic_vector(31 downto 0));
end component;

-- Register file inputs and outputs
signal RF_rAddr1 : std_logic_vector(4 downto 0);
signal RF_rAddr2 : std_logic_vector(4 downto 0);
signal RF_wAddr : std_logic_vector(4 downto 0);
signal RF_wD : std_logic_vector(31 downto 0);

```



```

signal RF_rD2 : std_logic_vector(31 downto 0);

-- 3. Data memory component
component data_memory
  port (
    address : in std_logic_vector(31 downto 0);
    write_data : in std_logic_vector(31 downto 0);
    clk : in std_logic;
    reset : in std_logic;
    MemWrite : in std_logic;
    MemRead : in std_logic;
    read_data : out std_logic_vector(31 downto 0));
end component;

-- Data memory output
signal DM_read_data : std_logic_vector(31 downto 0);

-- 4. Instruction memory component
component instruction_memory
  port (
    read_address : in std_logic_vector(31 downto 0);
    clk : in std_logic;
    reset: in std_logic;
    instruction : out std_logic_vector(31 downto 0));
end component;

-- Instruction memory output
signal IM_instruction : std_logic_vector(31 downto 0);

-- 5. Control unit component

```

```

component control_unit
port (
    opcode : in std_logic_vector(5 downto 0);
    RegDst : out std_logic;
    Branch : out std_logic;
    MemRead : out std_logic;
    MemtoReg : out std_logic;
    ALUOp : out std_logic_vector(1 downto 0);
    MemWrite : out std_logic;
    ALUSrc : out std_logic;
    RegWrite : out std_logic);
end component;

-- Control unit input and outputs
signal CU_opcode : std_logic_vector(5 downto 0);
signal CU_RegDst : std_logic;
signal CU_Branch : std_logic;
signal CU_MemRead : std_logic;
signal CU_MemtoReg : std_logic;
signal CU_ALUOp : std_logic_vector(1 downto 0);
signal CU_MemWrite : std_logic;
signal CU_ALUSrc : std_logic;
signal CU_RegWrite : std_logic;

-- 6. ALU Control unit component
component ALU_control
port (
    ALUOp : in std_logic_vector(1 downto 0);
    funct : in std_logic_vector(5 downto 0);
    operation : out std_logic_vector(3 downto 0));

```

```

end component;

    -- ALU Control unit output
signal ALUcu_operation : std_logic_vector(3 downto 0);

-- 7. PC component
component PC
port (
    PCin : in std_logic_vector(31 downto 0);
    reset : in std_logic;
    clk : in std_logic;
    PCout : out std_logic_vector(31 downto 0));
end component;

-- PC inputs and output
signal PC_PCin : std_logic_vector(31 downto 0);
signal PC_PCout : std_logic_vector(31 downto 0);

-- 8. Mux 2to1 5 bit component
component mux2to1_5bit
port (
    a1: in std_logic_vector(4 downto 0);
    a2: in std_logic_vector(4 downto 0);
    s : in std_logic;
    d: out std_logic_vector(4 downto 0));
end component;

-- 9. Sign extender component
component sign_extender
port (

```

```

    sin : in std_logic_vector(15 downto 0);
    sout: out std_logic_vector(31 downto 0));
end component;

-- Sign extender output
signal SE_sout: std_logic_vector(31 downto 0);

-- 10, 11, 12. Mux 2to1 32 bit component
component mux2to1_32bit
port (
    a1: in std_logic_vector(31 downto 0);
    a2: in std_logic_vector(31 downto 0);
    s : in std_logic;
    d: out std_logic_vector(31 downto 0));
end component;

-- 12. Mux 2to1 32 bit output
signal Mux2to132b_2s : std_logic;

-- 13. Shift left by 2 component
component shift_left2_32bit
port (
    sin : in std_logic_vector(31 downto 0);
    sout: out std_logic_vector(31 downto 0));
end component;

-- Shift left by 2 output
-- signal SL_sout: std_logic_vector(31 downto 0);

-- 14, 15. Adder component

```

```

component adder_32bit
port (
    a, b : in std_logic_vector(31 downto 0);
    cout: out std_logic_vector(31 downto 0));
end component;

-- Adder outputs
signal Add_cout: std_logic_vector(31 downto 0);
signal Add1_cout: std_logic_vector(31 downto 0);

begin

MIPS_clk <= clk;
MIPS_reset <= reset;

-- ALU
U1: ALU port map (
    D1 => ALU_D1,
    D2 => ALU_D2,
    operation => ALUcu_operation,
    alu_res => ALU_alu_res,
    zero => ALU_zero);

-- Register file
U2: register_file port map (
    rAddr1 => RF_rAddr1,
    rAddr2 => RF_rAddr2,
    wAddr => RF_wAddr,
    wD => RF_wD,
    RegWrite => CU_RegWrite,

```

```

    clk => MIPS_clk,
    reset => MIPS_reset,
    rD1 => ALU_D1,
    rD2 => RF_rD2);

    RF_rAddr1 <= IM_instruction(25 downto 21);
    RF_rAddr2 <= IM_instruction(20 downto 16);

-- Data memory
U3: data_memory port map (
    address    => ALU_alu_res,
    write_data => RF_rD2,
    clk        => MIPS_clk,
    reset      => MIPS_reset,
    MemWrite   => CU_MemWrite,
    MemRead    => CU_MemRead,
    read_data  => DM_read_data);

-- Instruction memory
U4: instruction_memory port map (
    read_address => PC_P Cout,
    clk         => MIPS_clk,
    reset       => MIPS_reset,
    instruction  => IM_instruction);

-- Control unit
U5: control_unit PORT MAP (
    opcode      => CU_opcode,
    RegDst      => CU_RegDst,
    Branch      => CU_Branch,

```

```

    MemRead => CU_MemRead,
    MemtoReg => CU_MemtoReg,
    ALUOp => CU_ALUOp,
    MemWrite => CU_MemWrite,
    ALUSrc => CU_ALUSrc,
    RegWrite => CU_RegWrite);

    CU_opcode <= IM_instruction(31 downto 26);

-- ALU Control unit
U6: ALU_control port map (
    ALUOp => CU_ALUOp,
    funct => IM_instruction(5 downto 0),
    operation => ALUcu_operation);

-- PC
U7: PC port map (
    PCin => PC_PCin,
    reset => MIPS_reset,
    clk => MIPS_clk,
    PCout => PC_PCout);

-- Register destination Mux 2to1 5 bit
U8: mux2to1_5bit port map (
    a1 => IM_instruction(15 downto 11),
    a2 => IM_instruction(20 downto 16),
    s => CU_RegDst, -- if 0 then a2 else a1
    d => RF_wAddr);

-- Sign extender

```

```

U9: sign_extender port map (
    sin => IM_instruction(15 downto 0),
    sout => SE_sout);

-- Muxs 2to1 32 bit
-- ALU source mux
U10: mux2to1_32bit port map (
    a1 => SE_sout,
    a2 => RF_rD2,
    s => CU_ALUSrc, -- if 0 then a2 else a1
    d => ALU_D2);

-- Memory to Register file mux
U11: mux2to1_32bit port map (
    a1 => DM_read_data,
    a2 => ALU_alu_res,
    s => CU_MemtoReg, -- if 0 then a2 else a1
    d => RF_wD);

-- Branch mux
U12: mux2to1_32bit port map (
    a1 => Add_cout,
    a2 => Add1_cout,
    s => Mux2to132b_2s, -- if 0 then a2 else a1
    d => PC_PCin);

-- And
Mux2to132b_2s <= (not ALU_zero) and CU_Branch;

```



```

-- -- Shift left by 2
-- U13: shift_left2_32bit port map (
--     sin => SE_sout,
--     sout => SL_sout);

-- Adders
U14: adder_32bit port map (
    a => PC_PCout,
    b => x"00000001",
    cout => Add1_cout);

U15: adder_32bit port map (
    a => Add1_cout,
    b => SE_sout,
    cout => Add_cout);

end structural;

```

➤ Testbench

Το testbench έχει ρολόι περιόδου 10 ns. Για τον έλεγχο πρώτα γίνεται reset για να μηδενιστούν τα δεδομένα των καταχωρητών και στη συνέχεια εκτελείται το πρόγραμμα. Ο χρόνος ο οποίος χρειάζεται για να εκτελεσθούν οι εντολές πριν την εντολή bne είναι 220 ns και στη συνέχεια το πρόγραμμα εκτελείται για 50 ns. Άρα συνολικά ο χρόνος εκτέλεσης είναι 280 ns.

- Κώδικας

```

library IEEE;
use IEEE.std_logic_1164.all;

```

```
entity MIPS_tb is
end MIPS_tb;
```

architecture test of MIPS_tb is

```
    component MIPS
    port (
        reset : in std_logic;
        clk : in std_logic
    );
    end component;

    -- inputs
    signal reset_tb : std_logic;
    signal clk_tb : std_logic;
```

```
begin
    U1: MIPS port map (
        reset => reset_tb,
        clk => clk_tb);
```

```
    -- clock process
    clk_p: process
    begin
        clk_tb <= '1';
        wait for 5 ns;
        clk_tb <= '0';
        wait for 5 ns;
```

```

end process clk_p;

-- stimulus process
process
begin

    reset_tb <= '1';
    wait for 10 ns;

    reset_tb <= '0';
    wait for 220 ns;

    -- branch not equal
    wait for 50 ns;

    -- runs for 280 ns

end process;
end test;

```

- **Αποτέλεσμα**

Στην εκτέλεση του testbench τα σήματα τα οποία εμφανίζονται είναι το reset, το ρολόι, η τρέχουσα εντολή, όλες οι θέσεις μνήμης του register file και οι θέσεις 0 έως 2 της μνήμης δεδομένων. Παρατηρούμε ότι το πρόγραμμα αποθηκεύει στους καταχωρητές 3 και 5 τους αριθμούς 1 και 3 αντίστοιχα. Στη συνέχεια αρχίζει η επανάληψη όπου στον καταχωρητή 6 αποθηκεύεται το περιεχόμενο του 3 και στη θέση της μνήμης δεδομένων με αριθμό το περιεχόμενο του καταχωρητή 4 αποθηκεύεται το περιεχόμενο του καταχωρητή 6. Στη συνέχεια της επανάληψης προθέτονται στους καταχωρητές 3, 4, και 5 οι αριθμοί 1, 1 και -1 αντίστοιχα. Αν ο καταχωρητής 5 δεν έχει τιμή ίση με 0 τότε συνεχίζεται η επανάληψη.

Στη πρώτη επανάληψη στο καταχωρητή 6 αποθηκεύεται ο αριθμός 1 και στη θέση 0 της μνήμης δεδομένων αποθηκεύεται το 1. Μετά από τις προσθήσεις οι καταχωρητές 3, 4 και 5 έχουν τις τιμές 2, 1

και 2. Ο καταχωρητής 5 δεν έχει τιμή ίση με 0 οπότε συνεχίζεται η επανάληψη. Στη δεύτερη επανάληψη στο καταχωρητή 6 αποθηκεύεται ο αριθμός 2 και στη θέση 1 της μνήμης δεδομένων αποθηκεύεται το 2. Μετά από τις προσθέσεις οι καταχωρητές 3, 4 και 5 έχουν τις τιμές 3, 2 και 1. Ο καταχωρητής 5 δεν έχει τιμή ίση με 0 οπότε συνεχίζεται η επανάληψη. Στη πρώτη τρίτη στο καταχωρητή 6 αποθηκεύεται ο αριθμός 3 και στη θέση 2 της μνήμης δεδομένων αποθηκεύεται το 3. Μετά από τις προσθέσεις οι καταχωρητές 3, 4 και 5 έχουν τις τιμές 4, 3 και 0. Ο καταχωρητής 5 έχει τιμή ίση με 0 οπότε τελειώνει η επανάληψη και τερματίζεται το πρόγραμμα.

